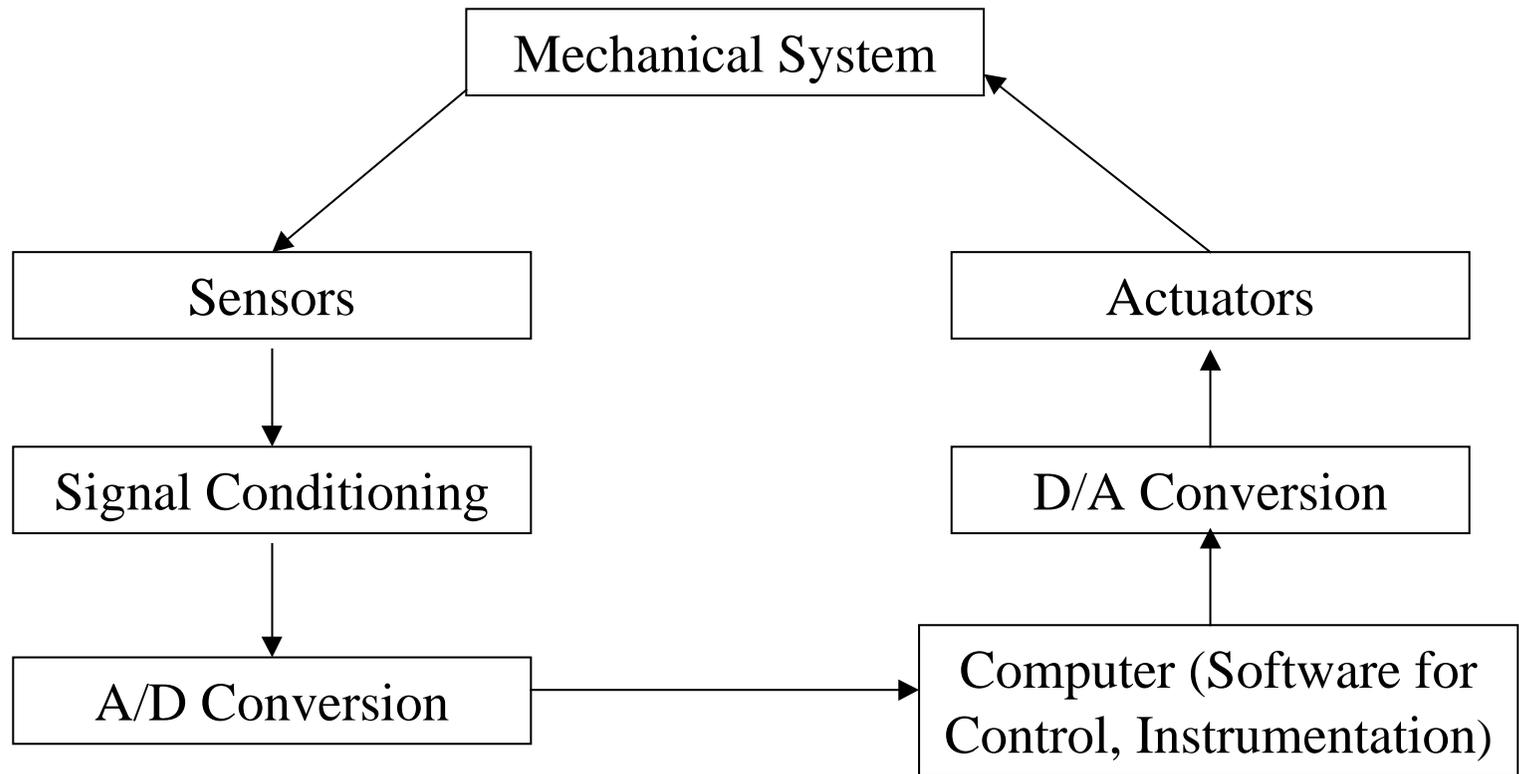


Purpose of ENGR 271


- * To introduce A/D and D/A conversion.
- * To work with sensors.
- * To introduce feedback control.


Mechatronic System



Digital Systems

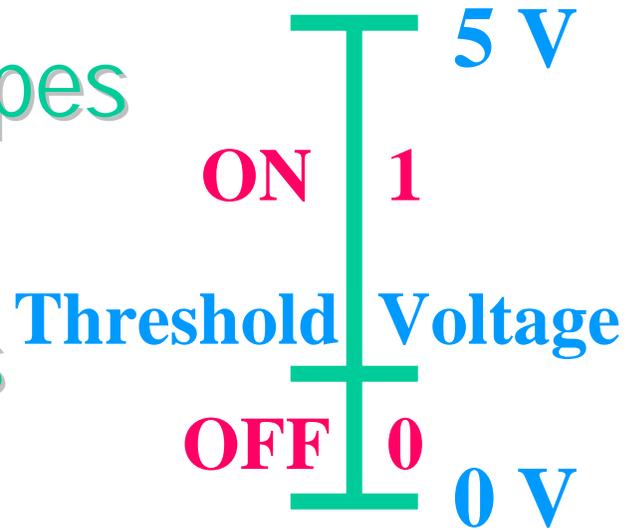- * Transistors "on" or "off," 5 V or 0 V.
- * Binary information, 0 or 1.
- * Digital meters and scopes
- * also depend on analog
- * "Mixed-signal" devices



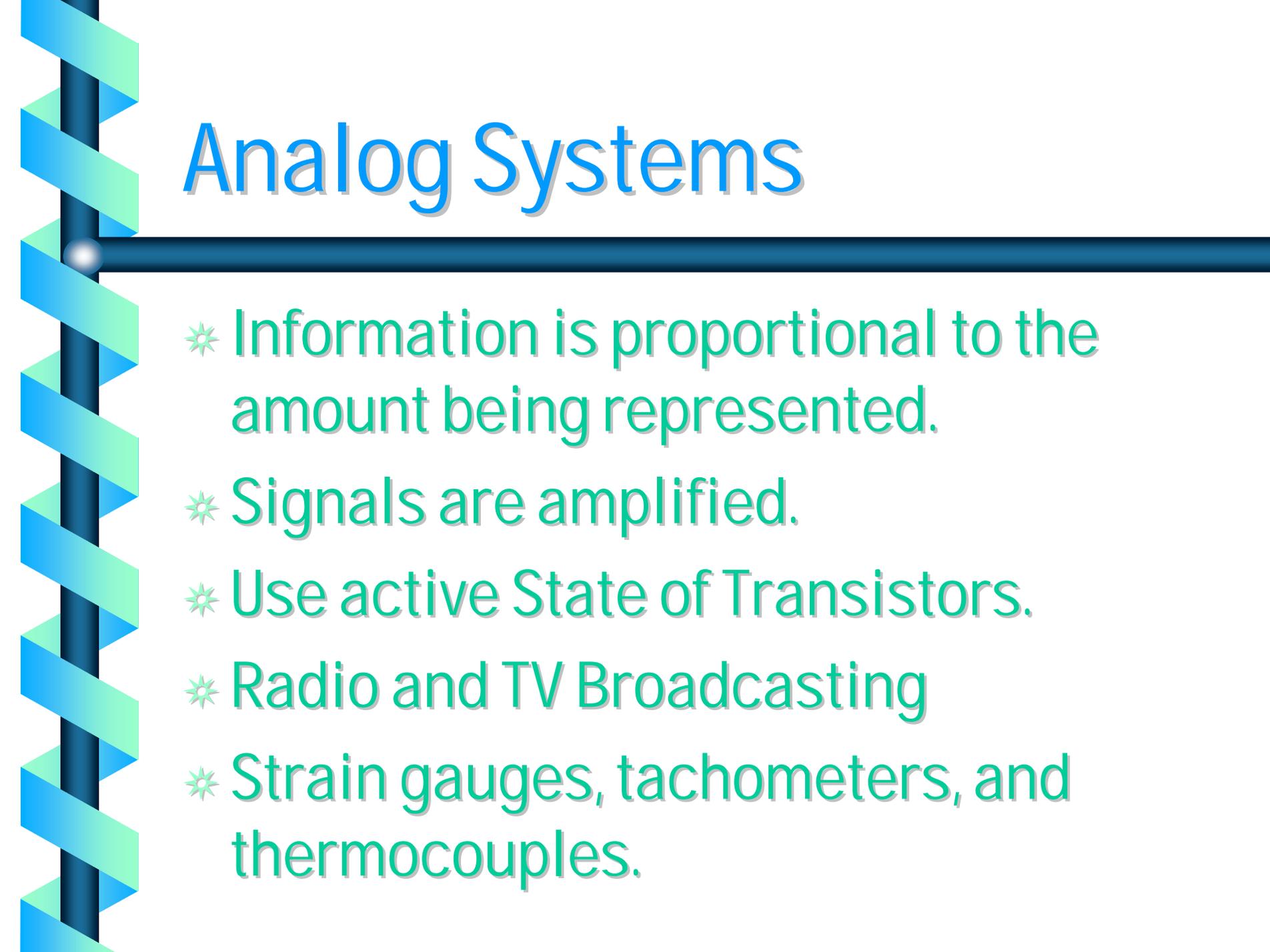


Analog Systems

- * Information is proportional to the amount being represented.
- * Signals are amplified.
- * Use active State of Transistors.
- * Radio and TV Broadcasting
- * Strain gauges, tachometers, and thermocouples.

LED Operation

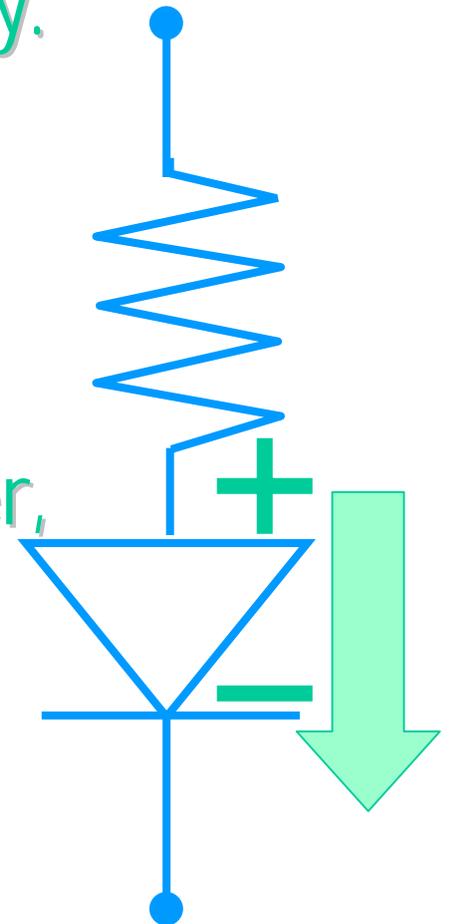- * Current through LED flows 1 way.
- * Current flows if anode (+)
- * is at a higher potential (V)
- * than cathode (-).
- * If voltage at the anode is higher,
- * then LED is reverse biased and
- * no current flows.



Ohm's Law

- * Current is inversely related to resistance.
- * Increase resistance, decrease current.


$$I = \frac{V}{R}$$

- * Voltage, V, in Volts (V)
- * Current, I, in Amperes (A)
- * Resistance, R, in ohms (Ω)

Potentiometer


- * Adjustable Resistance
- * $100k = R1 + R2$
- * $V1 + V2 = 5 V$
- * Voltage Divider:

$$V_2 = 5 \cdot \frac{R_2}{R_1 + R_2}$$

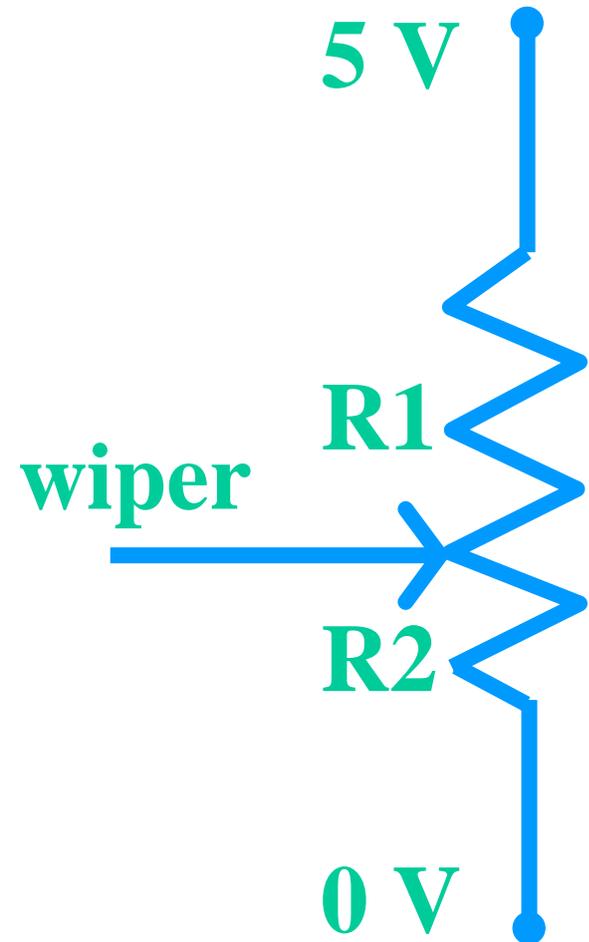


Op-Amp

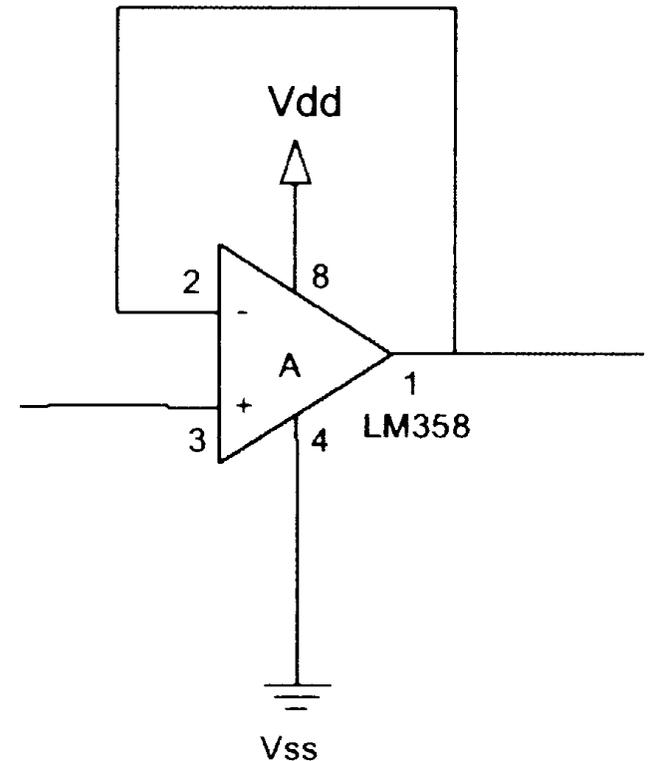- * "Active" device (needs power).
- * High-gain amplifier.
- * Also used as a filter,
- * comparator,
- * signal generator.



Voltage Follower

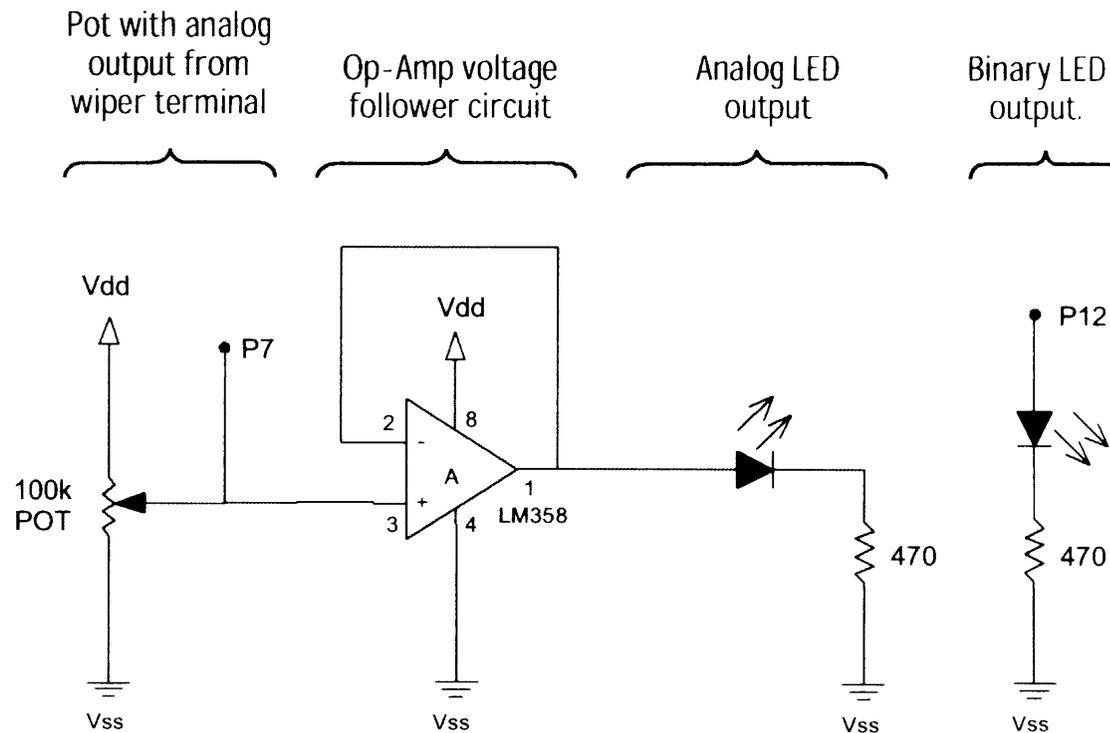* V_{out} follows V_{in} (i.e., $V_{out} = V_{in}$).



Comparator

$V_{\text{input}} > V_{\text{threshold}}$, then $V_{\text{output}} = V_{\text{high}}$

$V_{\text{input}} < V_{\text{threshold}}$, then $V_{\text{output}} = V_{\text{low}}$

